



Higher Physics - Unit 2



2.1 Electric fields and resistors in circuits



Electric Fields


Electric fields exist in the regions around electric charges.

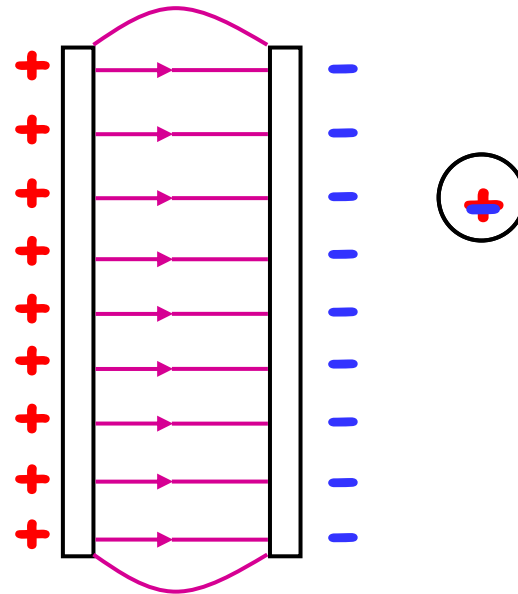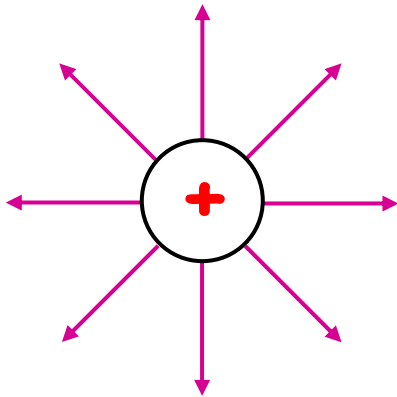A charge experiences a force in an electric field.



The arrows show the direction a positive charge will be forced to move.

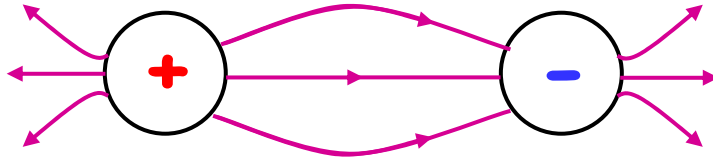When **two opposite charges** are close, we see:



Electric Fields and Conductors

On applying an **electric field** to a **conductor**, the **free electric charges** (electrons) **move**.

These free electric **charges moving**, are called an **electric current**.

Worksheet - Electricity & Electronics Tutorial

Q1 & Q2



Charges in Electric Fields

For a **charge** to move through an **electric field**, **work** must be done:

$$W = QV$$

work done
(or energy gained
by charge)
(J, Joules)

charge
(C, Coulombs)

potential
difference
(V, Volts)

The **potential difference** (V) between two points is a measure of the **work done** in **moving one coulomb of charge** between the points.

$$V = \frac{W}{Q}$$

Example 1

60 J of work is done moving a charge through a p.d. of 2 kV.

Calculate the size of the charge.

$$W = 60 \text{ J}$$

$$V = 2 \text{ kV}$$

$$= 2 \times 10^3 \text{ V}$$

$$Q = ?$$

$$W = Q V$$


$$Q = \frac{W}{V}$$

$$= \frac{60}{2 \times 10^3}$$

$$\underline{\underline{Q = 0.03 \text{ C}}}$$

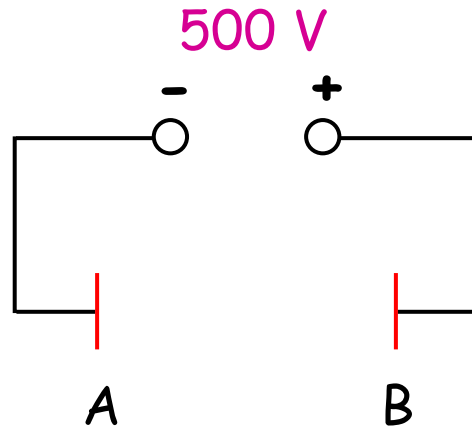Example 2

An electron is moved from plate A to plate B as shown.



Calculate the energy gained by the electron

$$V = 500 \text{ V}$$

$$Q_{\text{electron}} = 1.60 \times 10^{-19} \text{ C}$$

**** info from data sheet ****

$$W = ?$$

$$W = Q V$$

$$= (1.60 \times 10^{-19}) \times 500$$

$$\underline{\underline{W = 8 \times 10^{-17} \text{ J}}}$$

Example 3

An electron is moved between two metal plates with a potential difference of 5 kV.

Calculate the velocity of the electron as it reaches the positive plate.

$$\begin{aligned} V &= 5 \text{ kV} \\ &= 5 \times 10^3 \text{ V} \end{aligned}$$

$$Q_{\text{electron}} = 1.60 \times 10^{-19} \text{ C}$$

**** info from data sheet ****

$$W = ?$$

$$\begin{aligned} W &= Q V \\ &= (1.60 \times 10^{-19}) \times (5 \times 10^3) \\ \underline{\underline{W &= 8 \times 10^{-16} \text{ J}}} \end{aligned}$$

Energy is conserved.

$$E_k = W$$
$$= 8 \times 10^{-16} \text{ J}$$

$$m_{\text{electron}} = 9.11 \times 10^{-31} \text{ kg}$$

**** info from data sheet ****

$$v = ?$$

$$E_k = \frac{1}{2} m v^2$$

$$8 \times 10^{-16} = \frac{1}{2} \times (9.11 \times 10^{-31}) \times v^2$$

$$8 \times 10^{-16} = (4.555 \times 10^{-31}) \times v^2$$

$$v^2 = \frac{8 \times 10^{-16}}{4.555 \times 10^{-31}}$$

$$v^2 = 1.756 \times 10^{15}$$

$$v = \sqrt{1.756 \times 10^{15}}$$

$$v = \underline{\underline{41.9 \times 10^6 \text{ ms}^{-1}}}$$

Worksheet - Electricity & Electronics Tutorial

Q3 - Q7



Definition of a Volt

Consider the equation $W = Q V$.

Rearrange to give $V = \frac{W}{Q}$.

This means then that $1 \text{ Volt} = \frac{1 \text{ Joule}}{1 \text{ Coulomb}}$

This is written as: $1 \text{ V} = 1 \text{ J C}^{-1}$


Definition of 1 Volt

The potential difference between two points is **1 volt** when **1 Joule** of energy is required to **move 1 Coulomb** of charge between the two points.

Circuits with Batteries or Cells

Experiment

Set up the circuit shown.

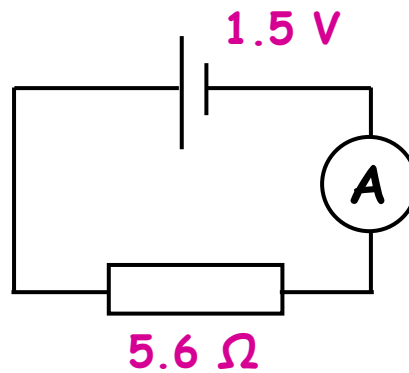

Calculation of Current in Circuit

$$V = 1.5 \text{ V}$$

$$R = 5 \Omega$$

$$I = ?$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$= \frac{1.5}{5}$$

$$\underline{\underline{I = 0.3 \text{ A}}}$$

Measurement of Current in Circuit

The reading on the ammeter is _____ A.

Why are the two results different?

Answer

The results are different because the battery has a resistance inside it, which we have not taken into consideration previously.


This resistance is called the **INTERNAL RESISTANCE** of the battery and has the symbol **r** .

Internal Resistance

Every **electrical source** can be thought of as a **source of emf** with a **resistor in series**.

The resistance from within a cell or battery is known as **INTERNAL RESISTANCE**.

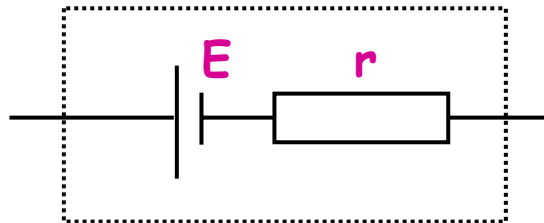
Batteries or cells with internal resistance should be drawn as shown.



Measuring emf of a Battery

Experiment

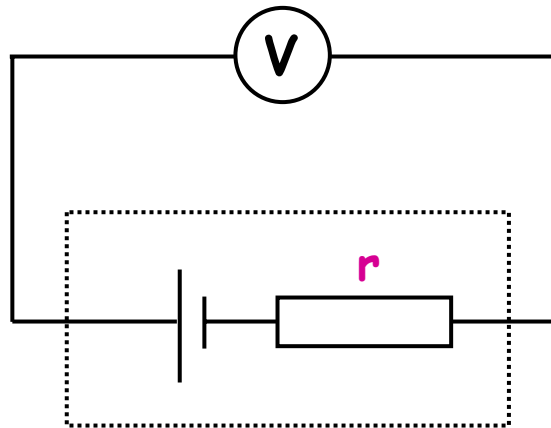Connect a voltmeter across the terminals of a battery as shown.



Reading on \textcircled{V} = emf.

The nominal emf of a battery is usually written on it.

(e.g. an AA battery has an emf of 1.5 V, however checking this with a voltmeter may give about 1.54 V)



Electromotive Force (emf)


The **maximum voltage** of a battery is called the electromotive force (**emf**) and has the symbol **E**.

The emf of an electrical supply is:

the number of Joules of energy given to each Coulomb of charge passing through the supply.

Remember: $1\text{ V} = 1\text{ J C}^{-1}$

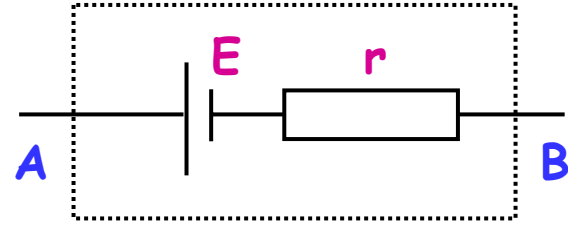The **voltage** measured across the **cell** is measured between terminals **A** and **B**.



This is called the **TERMINAL POTENTIAL DIFFERENCE** (tpd).

When the **circuit** is **open**, **no current** is being taken from the source, and so **no energy** is **lost** in overcoming the internal resistance.

This means:


e.m.f. of a source = open circuit t.p.d.


Example 1

A battery of emf 1.5 V and internal resistance $0.5\ \Omega$, is connected to a $6\ \Omega$ resistor.

(a) Calculate the current in the circuit.

Draw diagram and insert values given.

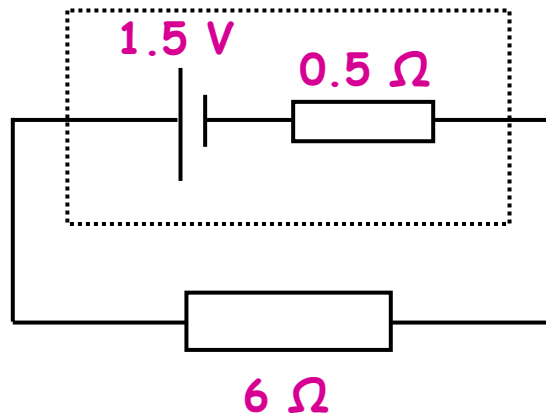

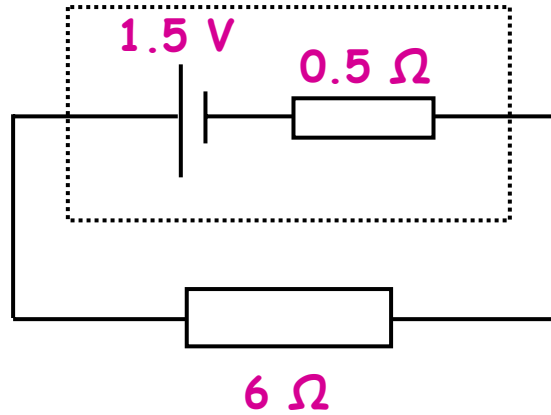

$$V = 1.5 \text{ V}$$

$$r = 0.5 \Omega$$

$$R = 6 \Omega$$

$$R_{\text{tot}} = 6.5 \Omega$$

$$I = ?$$


$$V = I R_{\text{tot}}$$

$$I = \frac{V}{R_{\text{tot}}}$$

$$= \frac{1.5}{6.5}$$

$$I = \underline{\underline{0.23 \text{ A}}}$$

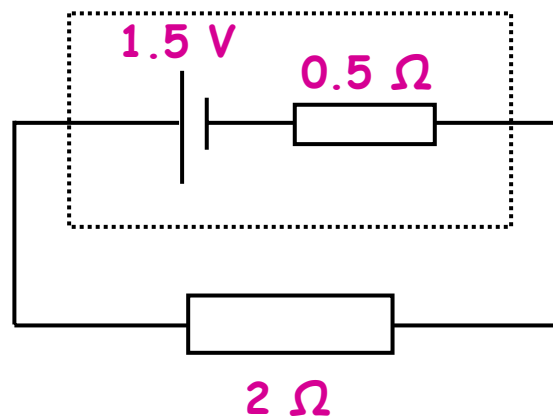- (b) The $6\ \Omega$ resistor is replaced by a $2\ \Omega$ resistor.
Calculate the new current in the circuit.



$$V = 1.5\text{ V}$$

$$r = 0.5\ \Omega$$

$$R = 2\ \Omega$$

$$R_{\text{tot}} = 2.5\ \Omega$$

$$I = ?$$

$$V = I R_{\text{tot}}$$


$$I = \frac{V}{R_{\text{tot}}}$$

$$= \frac{1.5}{2.5}$$

$$I = \underline{\underline{0.6\text{ A}}}$$

- (c) The battery is short circuited using thick copper wire, which has negligible resistance.

Calculate the short circuit current.

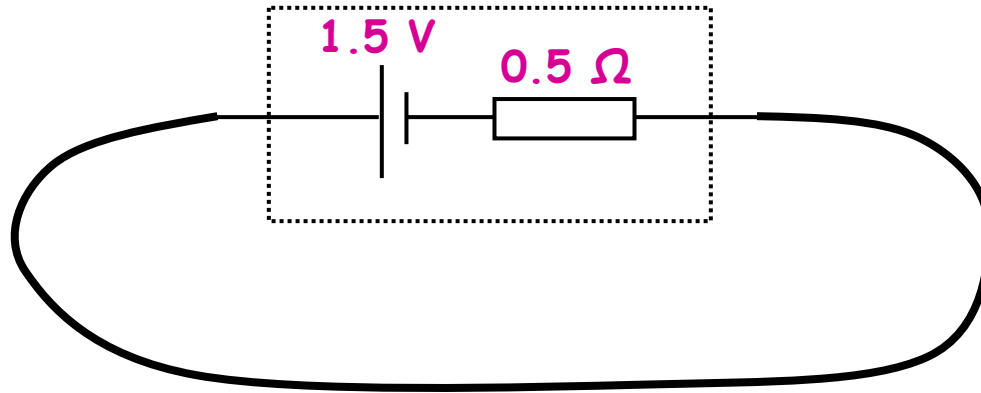

$$V = 1.5 \text{ V}$$

$$R_{\text{tot}} = 0.5 \Omega$$

$$I = ?$$


$$I = \frac{V}{R_{\text{tot}}}$$

$$= \frac{1.5}{0.5}$$

$$I = \underline{\underline{3 \text{ A}}}$$


emf and Internal Resistance

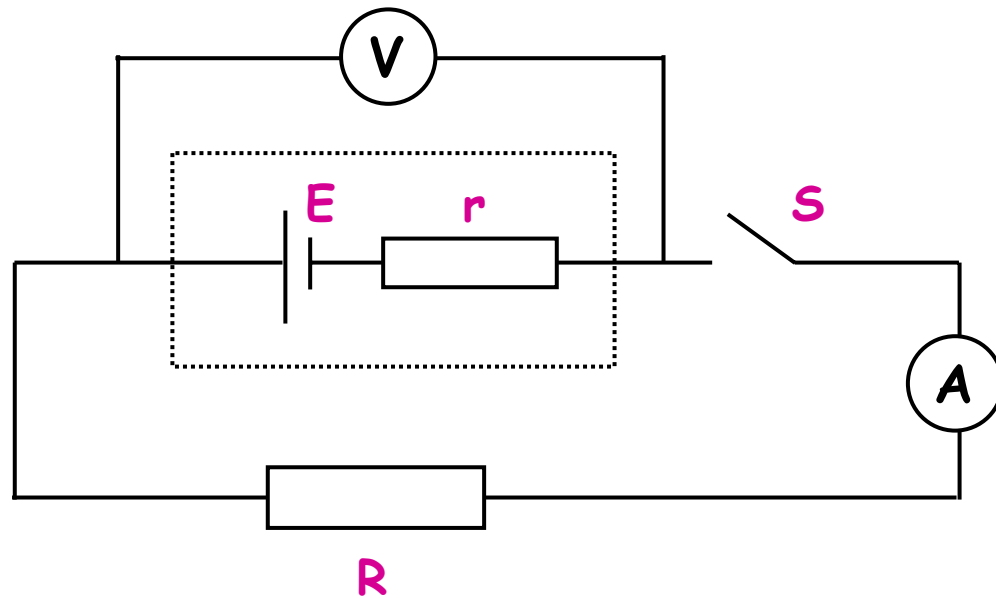The following circuit is used to find the emf and internal resistance of a cell.



Switch S Open

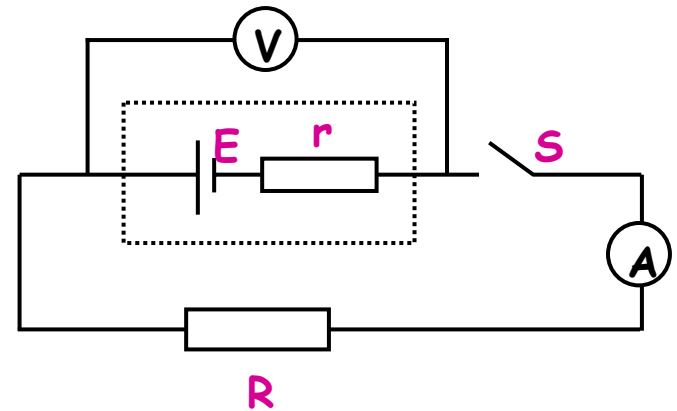- reading on \textcircled{V} = emf
- reading on \textcircled{A} = 0 A



Switch S Closed

- reading on \textcircled{V} falls to a value less than emf.
- the reading now on \textcircled{V} is called the **TERMINAL POTENTIAL DIFFERENCE**.
- the **tpd** is the **voltage** across the **external resistor R**.
- voltage across internal resistance of the battery = emf - tpd.
- this voltage is called **LOST VOLTS** (voltage used up overcoming internal resistance).

The 'lost volts' increase with current.

This gives us the following relationship:

$$\text{emf} = \text{tpd} + \text{lost volts}$$


The diagram shows the equation $E = IR + Ir$ enclosed in a red rectangular box. Each term (E , IR , and Ir) is circled with a dashed pink line. Dotted pink lines connect these terms to labels: 'emf (V)' points to E , 'tpd (V)' points to IR , and 'lost volts (V)' points to Ir .

In the SQA data book, the equation is given as:

$$E = V + Ir$$

Internal Resistance Problems

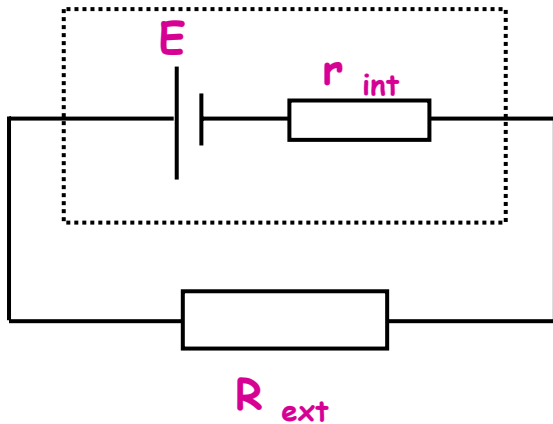Ohm's Law, $V = IR$ applies to ALL circuits, as does the fact that voltages in a series circuit add up to give the supply voltage.



emf = total voltage


tpd = voltage across R_{ext}

lost volts = voltage across r_{int}

Example 1

A cell with emf 2 V and internal resistance 0.75Ω is connected to an external resistor of 3Ω .

(a) Draw a circuit diagram.

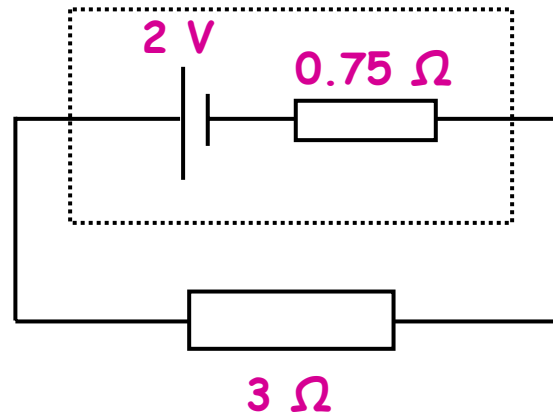

(b) Calculate the current in the circuit.

$$E = 2 \text{ V}$$

$$R = 3 \Omega$$

$$r = 0.75 \Omega$$

$$I = ?$$

$$E = IR + Ir$$

$$E = I(R + r)$$

$$2 = I(3 + 0.75)$$

$$3.75 I = 2$$

$$\underline{\underline{I = 0.53 \text{ A}}}$$

(c) Calculate the lost volts.

**** Lost volts is due to the internal resistance, so use r . ****

$$I = 0.53 \text{ A}$$

$$r = 0.75 \Omega$$

$$\text{lost volts} = ?$$

$$\text{lost volts} = Ir$$

$$= 0.53 \times 0.75$$

$$\text{lost volts} = \underline{\underline{0.4 \text{ V}}}$$

(d) Calculate the terminal potential difference.

**** tpd is voltage across the external resistor, so use R. ****

$$I = 0.53 \text{ A}$$

$$R = 3 \Omega$$

$$\text{tpd} = ?$$

$$\text{tpd} = I R$$

$$= 0.53 \times 3$$

$$\underline{\underline{\text{tpd} = 1.6 \text{ V}}}$$

An alternate method:

$$\text{emf} = \text{tpd} + \text{lost volts}$$

$$\text{tpd} = \text{emf} - \text{lost volts}$$

$$= 2 - 0.4$$

$$\underline{\underline{\text{tpd} = 1.6 \text{ V}}}$$

Worksheet - Electricity & Electronics Tutorial

Q15, Q16, Q17, Q18, Q19*, Q20, Q21*,
Q22 - Q24.

Worksheet - Internal Resistance


Q1 - Q6.

Measuring emf & Internal Resistance

Experiment (Method 1)

The circuit shown is used to measure the emf and tpd

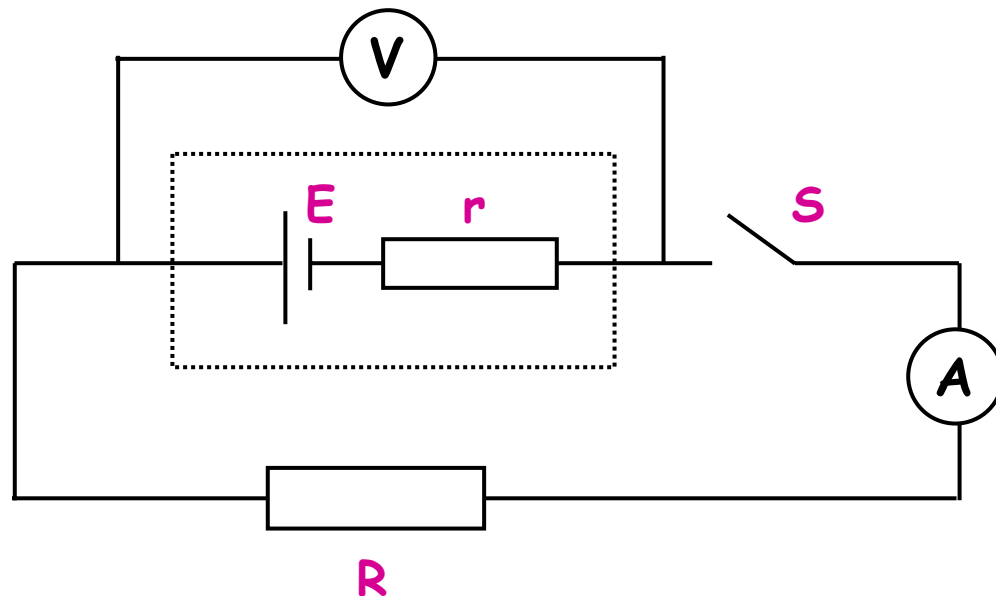The lost volts and internal resistance can then be calculated.



Switch S Open

voltmeter reading = _____ V

\therefore emf = _____ V

Switch S Closed

voltmeter reading = _____ V

\therefore tpd = _____ V

Calculation of Lost Volts

lost volts = emf - tpd

=

lost volts = _____ V

Calculation of Internal Resistance

$$I = \text{_____} A$$


$$r = \frac{\text{lost volts}}{I}$$

$$= \frac{\text{emf} - \text{tpd}}{I}$$

$$r = \text{_____} \Omega$$

Experiment (Method 2)

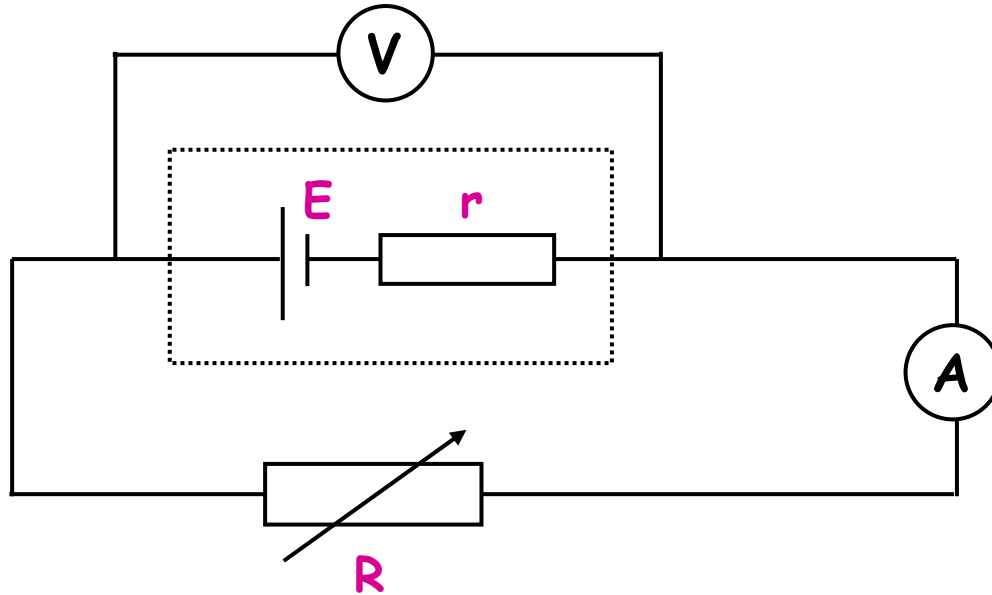The following circuit is used to measure internal resistance of a cell.



V measures the tpd V .

A measures the current I .

Record these values in a table of results.

Change the setting on the variable resistor and note the new values of V and I each time.

Repeat this several times.


Results

| <u>V (volts)</u> | <u>I (amps)</u> |
|-------------------------------|------------------------------|
| | |

Graph

Plot a graph of V against I .



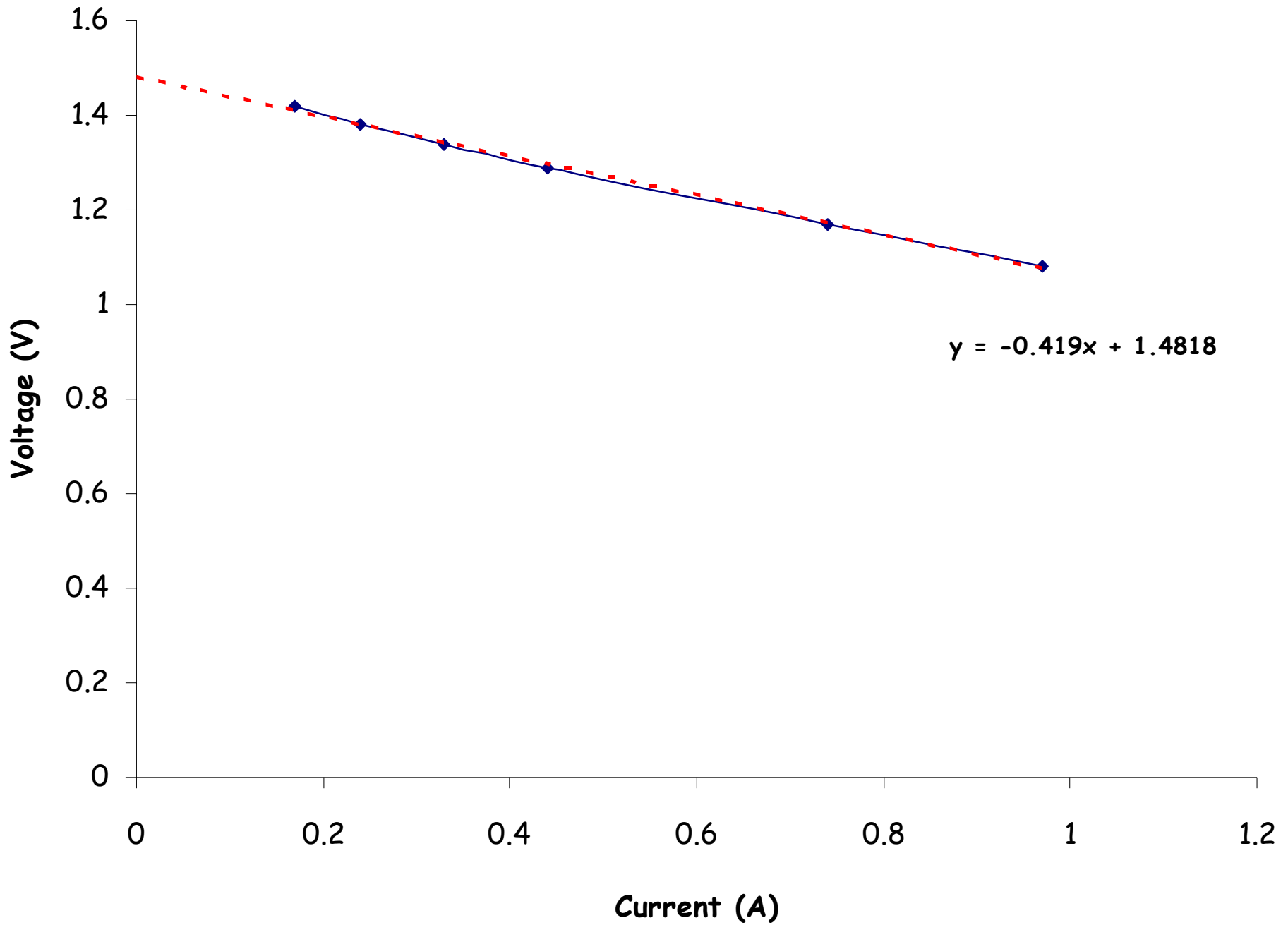

Theory

$$\text{emf} = \text{tpd} + \text{lost volts}$$

$$E = V + I r$$

$$V = E - I r$$

$$V = -r I + E$$

Compare this with the equation of a straight line: $y = m x + c$

$$r = |\text{gradient of graph}|$$


$$E = \text{intercept on } V \text{ axis}$$

To calculate the gradient of the graph: $\text{gradient} = \frac{V_2 - V_1}{I_2 - I_1}$

The internal resistance of the battery is _____ Ω .

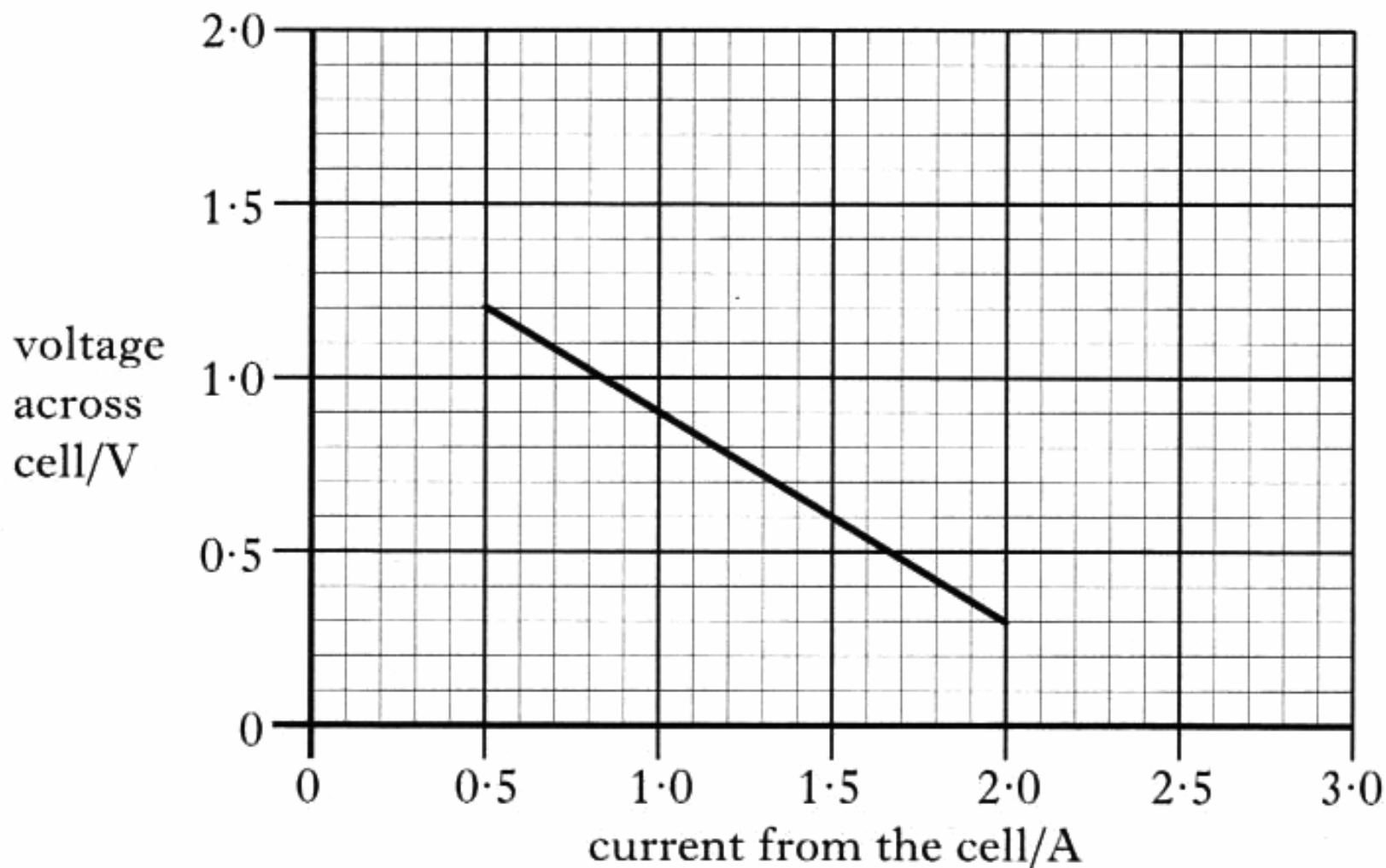Q1. *Adapted from Higher Physics SQP [X069/301]*

During an experiment to measure the e.m.f. and internal resistance of a cell, the following graph is obtained.



(a) Draw a circuit which could be used to obtain the data for this graph. (2)

(b) (i) What is the value of the e.m.f of the cell?

(ii) Calculate the internal resistance of the cell. (3)

Worksheet - Electricity & Electronics Tutorial

Q23, Q24



Conservation of Energy

Electromotive Force


When a **circuit** is **open** (no current flowing) the **pd across the terminals** is in fact the **emf**.

When a **current flows** through components, the **sum** of the **energies** produced in **each component equals** the **total energy** provided by the source.

$$\text{emf of closed circuit} = \text{sum of pd's across components}$$

Resistors in Series

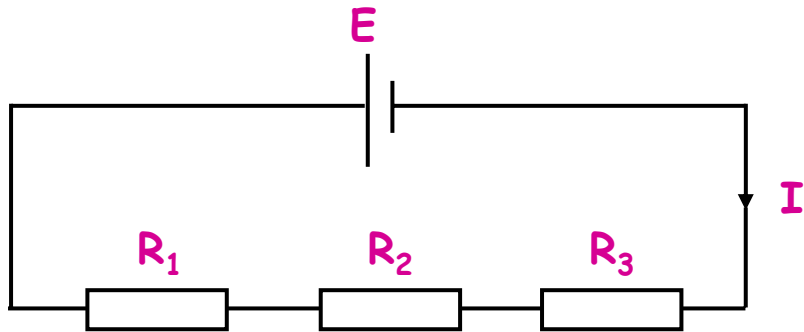The energy lost from the electrical source E , is gained by each of the resistors in series.



energy lost = energy gained

$$E = V_1 + V_2 + V_3$$

$$I R_T = I R_1 + I R_2 + I R_3$$


since current same at all points in a series circuit

$$R_T = R_1 + R_2 + R_3$$

Conservation of Charge

Resistors in Parallel

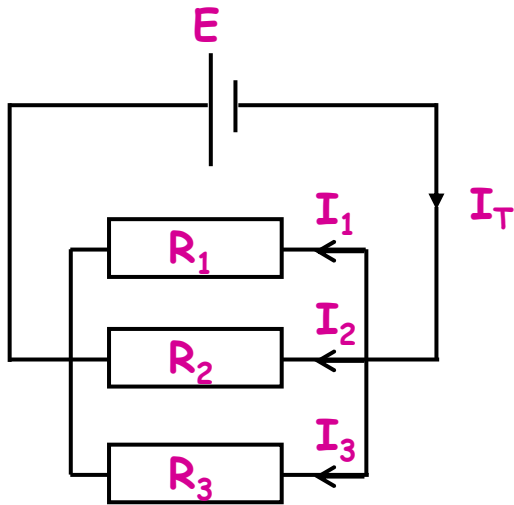The current (charge per second) splits up in a parallel circuit.



$$I_T = I_1 + I_2 + I_3$$

$$\frac{E}{R_T} = \frac{E}{R_1} + \frac{E}{R_2} + \frac{E}{R_3}$$

since voltage across each resistor constant and equal to supply

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Resistance Calculations

Calculations involving resistors will require you to **add resistors**, some in **parallel** and some in **series**.


Example 1

The circuit shows resistors connected as a potential divider.

Calculate the voltmeter reading:

(a) when the switch S is open

(b) when the switch S is closed.

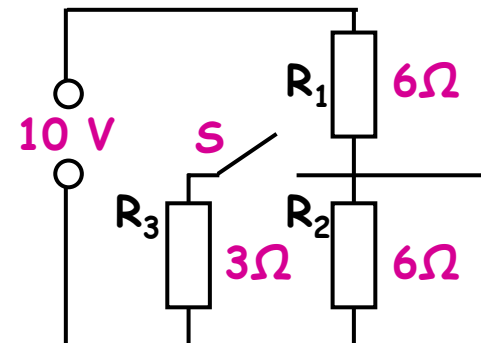

(a)

**** Switch S open, so have a series circuit with two resistors ****

$$R_1 = 6 \Omega$$

$$R_2 = 6 \Omega$$

$$V_T = 10 \text{ V}$$

$$R_T = R_1 + R_2$$

$$= 6 + 6$$

$$\underline{\underline{R_T = 12 \Omega}}$$

Know **total voltage**, and **total resistance**, so can calculate **total current**.

$$I_T = \frac{V_T}{R_T}$$

$$= \frac{10}{12}$$

$$\underline{\underline{I_T = 0.83 \text{ A}}}$$

**** Series circuit, \therefore total current must flow through each resistor. ****

$$I_T = 0.83 \text{ A}$$

$$R = 6 \Omega$$

$$V = ?$$

$$V = IR$$

$$= 0.83 \times 6$$

$$\underline{\underline{V = 5 \text{ V}}}$$

(b) **** Switch closed, two resistors in parallel now. ****

$$R_2 = 6 \Omega$$

$$R_3 = 3 \Omega$$

$$R_p = ?$$

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3}$$


$$= \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_p} = 0.5$$



$$R_p = \frac{1}{0.5}$$

$$\underline{\underline{R_p = 2 \Omega}}$$

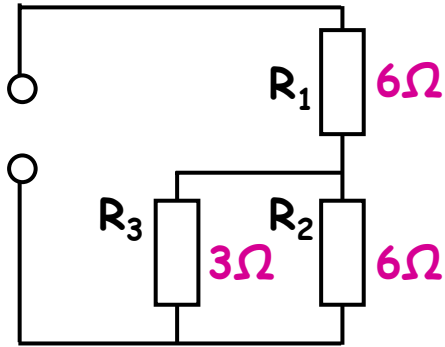**** Now have two resistors in series. ****



Combined R_2 and R_3 .

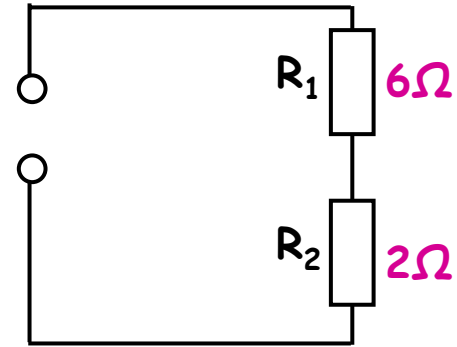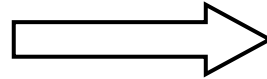

Now need to combine these resistors to find total resistance.

$$R_1 = 6 \Omega$$

$$R_2 = 2 \Omega$$

$$V_T = 10 \text{ V}$$

$$R_T = R_1 + R_2$$

$$= 6 + 2$$

$$\underline{\underline{R_T = 8 \Omega}}$$

Know **total voltage**, and **total resistance**, so can calculate **total current**.

$$I_T = \frac{V_T}{R_T}$$

$$= \frac{10}{8}$$

$$\underline{\underline{I_T = 1.25 \text{ A}}}$$

So can now calculate the size of voltage across R_1 .

$$R_1 = 6 \Omega$$

$$I = 1.25 \text{ A}$$

$$V_1 = ?$$

$$V_1 = I R_1$$

$$= 1.25 \times 6$$


$$\underline{\underline{V_1 = 7.5 \text{ V}}}$$

The voltage across R_2 is given by: $10 - 7.5 = \underline{\underline{2.5 \text{ V}}}$

Voltage across R_3 is also 2.5 V (voltage across components in parallel are same).

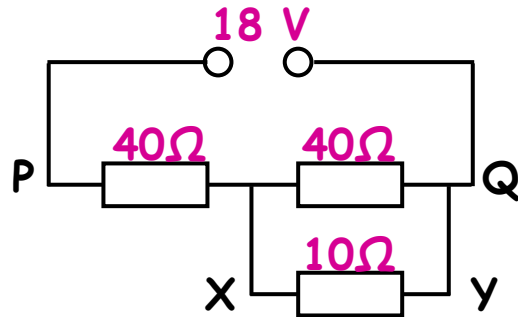Example 2

A potential divider, PQ is set up as shown.



Calculate the potential difference across XY.

**** Add the two resistors in parallel. ****

$$R_1 = 40 \Omega$$

$$R_2 = 10 \Omega$$

$$R_p = ?$$




$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{40} + \frac{1}{10}$$

$$\frac{1}{R_p} = 0.125$$

$$\underline{\underline{R_p = 8 \Omega}}$$

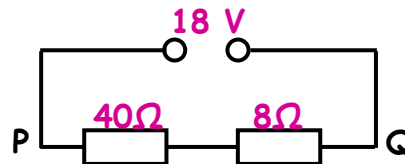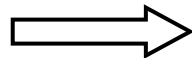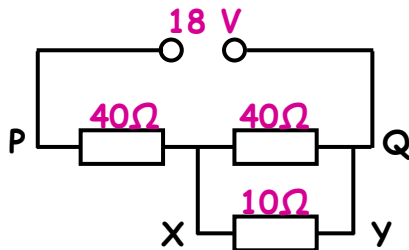**** Now have two resistors in series, 8Ω and 40Ω . ****



$$R_T = 8 + 40$$

$$\underline{\underline{R_T = 48 \Omega}}$$

Know total voltage, and total resistance, so can calculate total current.

$$I_T = \frac{V_T}{R_T}$$

$$= \frac{18}{48}$$

$$\underline{\underline{I_T = 0.375 A}}$$

So the voltage across 40Ω is:

$$R = 40 \Omega$$

$$I = 0.375 A$$

$$V = ?$$

$$V = IR$$

$$= 0.375 \times 40$$


$$\underline{\underline{V = 15 V}}$$

So the voltage across each of the resistors in parallel is:

$$18 - 15 = \underline{\underline{3 V}}$$

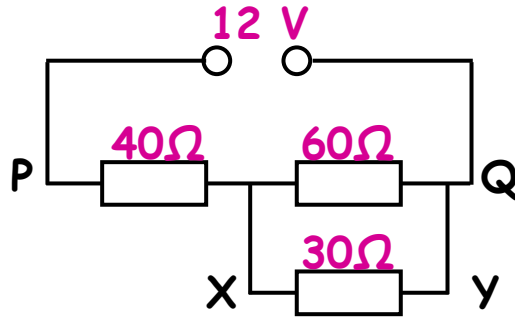Question

Calculate the potential difference across XY for the circuit shown.




potential difference across XY = 4 V

Worksheet - Electricity & Electronics Tutorial

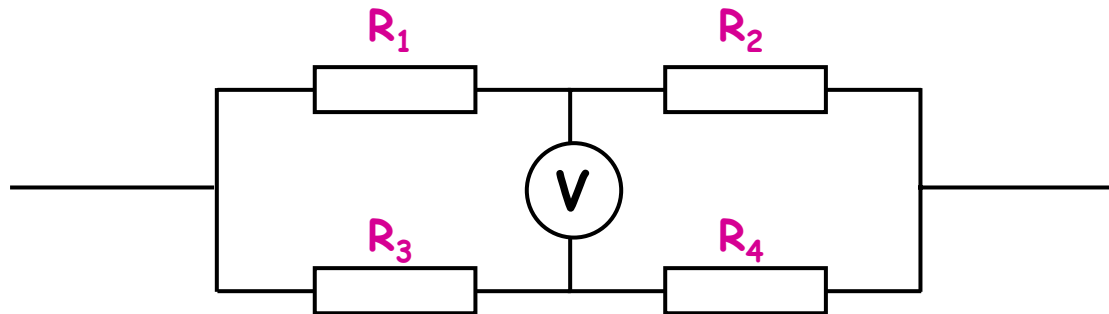Q11, Q12, Q13, Q14

Wheatstone Bridge

A *Wheatstone bridge* contains four resistors as shown.






The *bridge* is said to be *balanced* when the reading on $V = 0$ V.

When this is the case:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

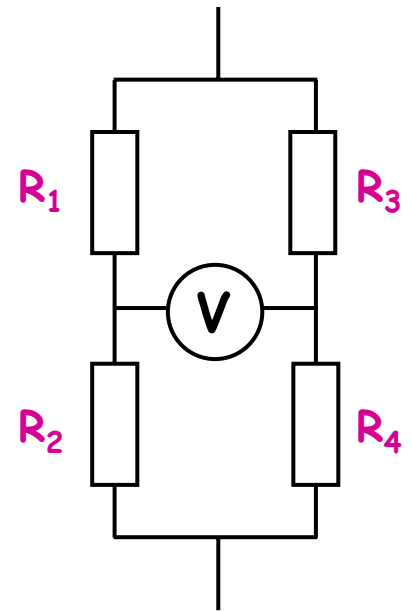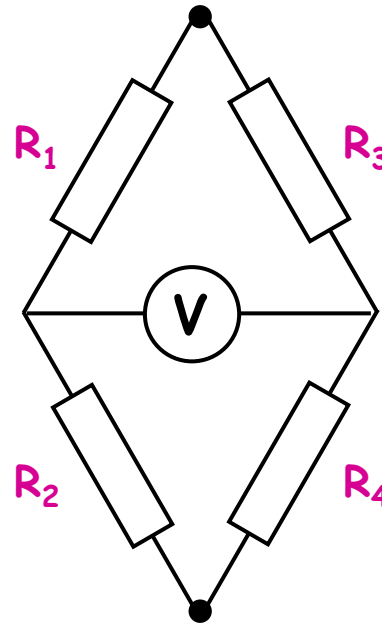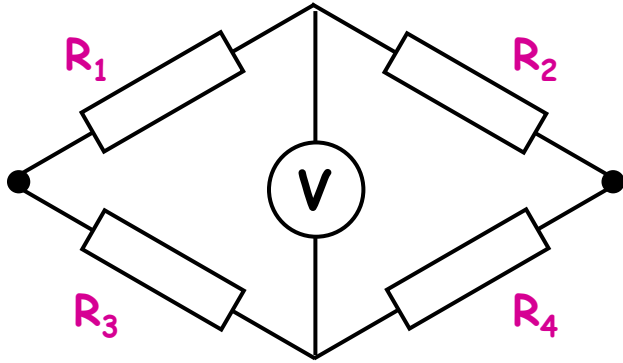Wheatstone bridge circuits are sometimes drawn:




Take care in numbering the resistors.

Resistors in *series* are *numbered consecutively*.

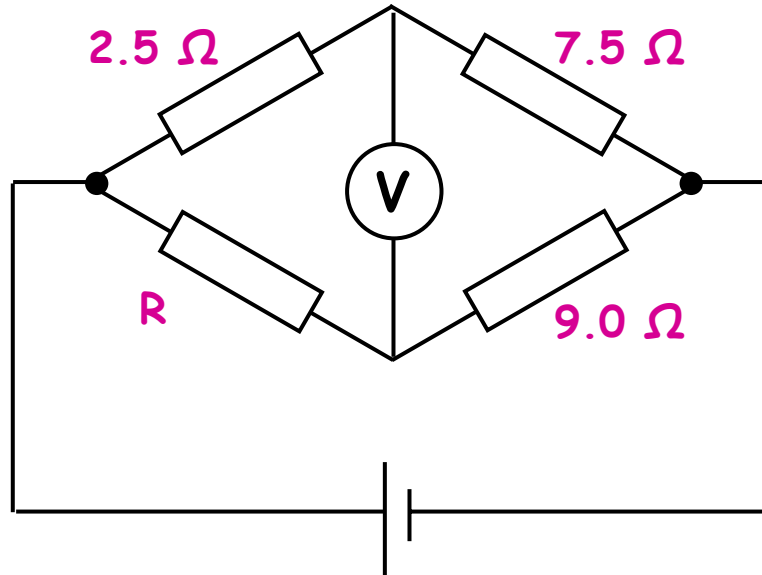Example 1 (Higher 2000 - A - Q9)

In the following circuit the reading on the voltmeter is zero.



The resistance of resistor R is

- A 0.33Ω
- B 0.48Ω
- C 2.1Ω
- D 3.0Ω
- E 27Ω

Balanced Wheatstone bridge $\Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$R_1 = 2.5 \Omega$$

$$R_2 = 7.5 \Omega$$

$$R_3 = ?$$

$$R_4 = 9.0 \Omega$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\frac{2.5}{7.5} = \frac{R}{9.0}$$


$$7.5 \times R = 2.5 \times 9.0$$

$$R = \frac{22.5}{7.5}$$

$$\underline{\underline{R = 3.0 \Omega}}$$

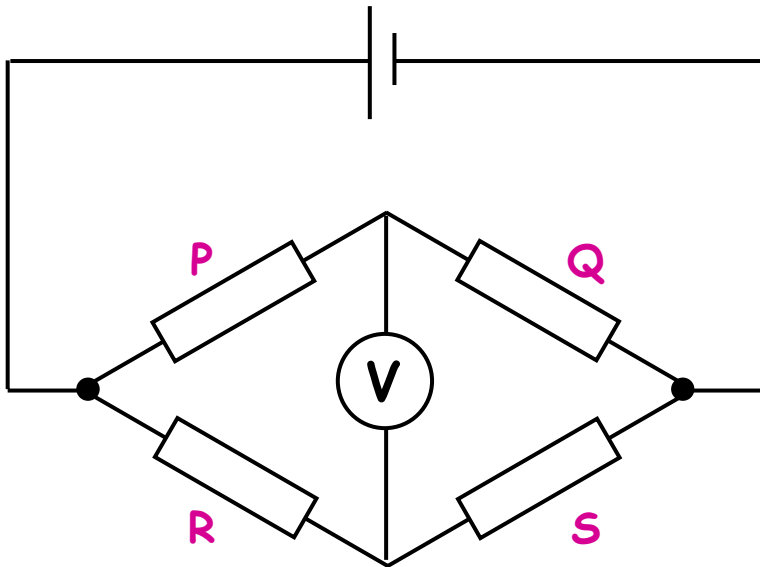Question (Higher 2002 - A - Q9)

The diagram below shows a balanced Wheatstone bridge where all the resistors have different values.



Which change(s) would make the bridge unbalanced?

- I. Interchange resistors P and S.
- II. Interchange resistors P and Q
- III. Change the e.m.f. of the battery.

A. I only

B. II only

C. III only

D. II and III only

E. I and III only

Consider

$$R_1 = 3 \Omega$$

$$R_2 = 5 \Omega$$

$$R_3 = 6 \Omega$$

$$R_4 = 10 \Omega$$

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{3}{5} = \frac{6}{10}$$

both sides = 0.6

\therefore balanced

I - interchange P and S

$$\frac{10}{5} = \frac{6}{3}$$

both sides = 2

\therefore balanced

II - interchange P and Q

$$\frac{5}{3} = \frac{6}{10}$$

both sides \neq same


\therefore unbalanced

Unbalanced Wheatstone Bridge

The **voltmeter** reading is **non-zero** when the Wheatstone Bridge is **unbalanced**.

To calculate voltmeter reading, use:
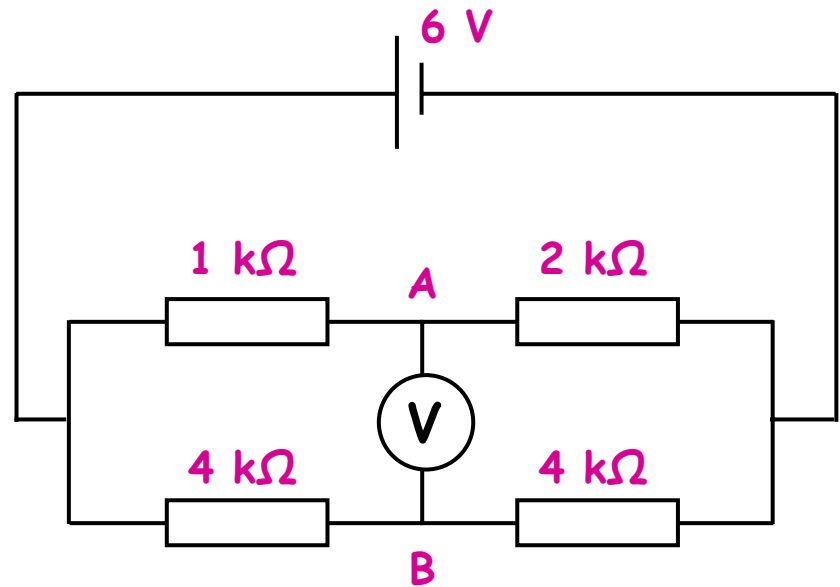
$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) \times V_S$$



Calculate the reading on the voltmeter (potential difference between A and B).

Potential Across R_1

$$R_1 = 1 \text{ k}\Omega$$

$$R_2 = 2 \text{ k}\Omega$$

$$V_s = 6 \text{ V}$$

$$V_2 = ?$$

$$V_2 = \left(\frac{R_2}{R_1 + R_2} \right) \times V_s$$

$$= \left(\frac{2}{2+1} \right) \times 6$$

$$\underline{\underline{V_2 = 4 \text{ V}}}$$

Potential Across R_2

$$R_3 = 4 \text{ k}\Omega$$

$$R_4 = 4 \text{ k}\Omega$$

$$V_s = 6 \text{ V}$$

$$V_4 = ?$$

$$V_4 = \left(\frac{R_4}{R_3 + R_4} \right) \times V_s$$

$$= \left(\frac{4}{4+4} \right) \times 6$$

$$\underline{\underline{V_4 = 3 \text{ V}}}$$

$$\begin{aligned} \text{potential difference between A and B} &= 4 - 3 \\ &= \underline{\underline{1 \text{ V}}} \end{aligned}$$


Relationship

In a balanced Wheatstone bridge circuit, $V = 0 \text{ V}$.

If any resistor is changed by ΔR , the bridge becomes unbalanced, meaning $V \neq 0 \text{ V}$.


We find that:

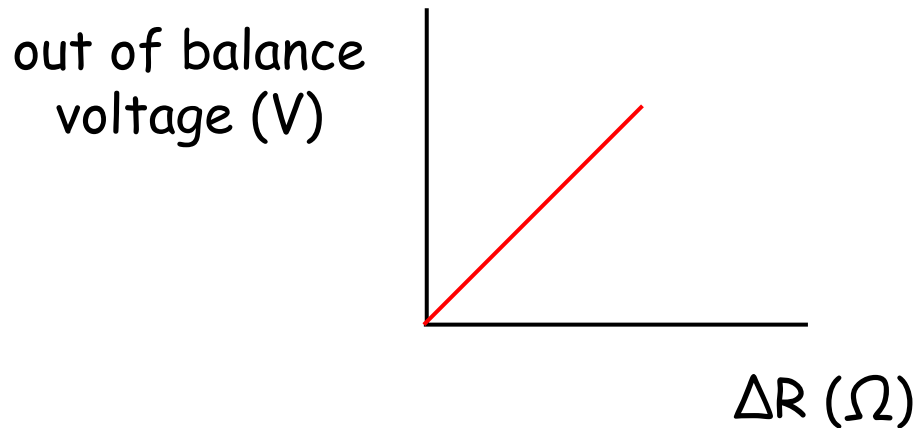out of balance voltage $\propto \Delta R$



Thermometer

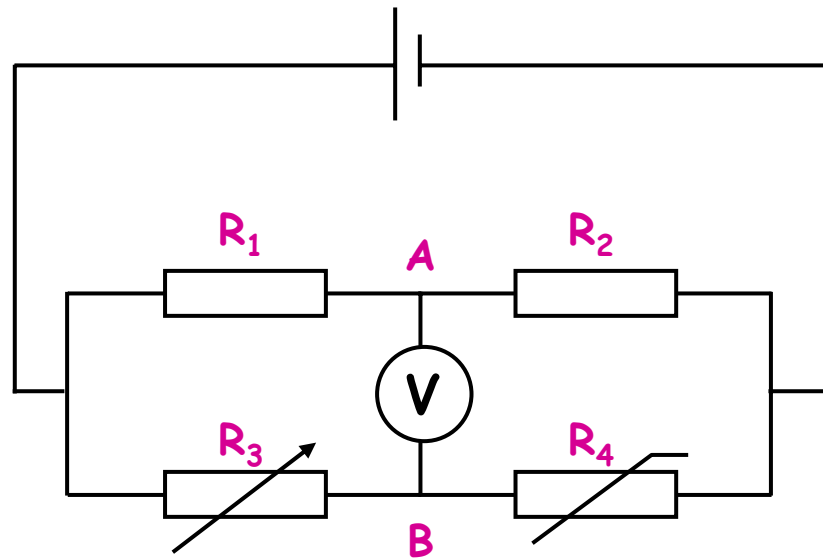A thermometer can be made using a Wheatstone Bridge circuit.



R_3 is a variable resistor.

R_4 is a thermistor (its resistance changes with temperature).

The bridge is balanced by adjusting the variable resistor.

When the bridge is balanced, $\text{V} = 0 \text{ V}$.

The scale is calibrated to read $^{\circ}\text{C}$ rather than volts.

As the thermistor is heated or cooled, the bridge becomes unbalanced.

This causes the temperature reading to change accordingly.

