



# Higher Physics - Unit 2

---


## 2.2 Alternating Current and Voltage


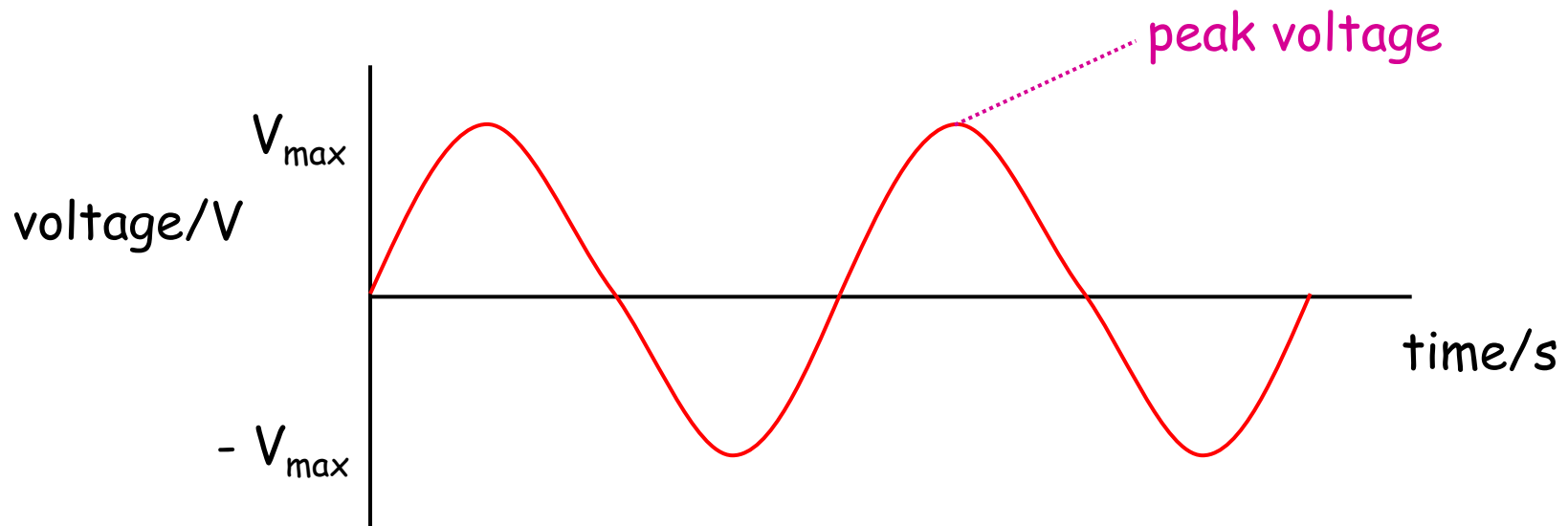
# AC Voltage Supply

---

The size of an AC voltage supply is constantly changing.



The maximum voltage is called the peak voltage,  $V_p$ .

Since the size of the voltage is changing, we use an **average value** when doing **calculations**.

The average value used is the "**root mean square**" or rms voltage.

It is calculated using:

$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}}$$

The **rms voltage equals** the equivalent **dc voltage**.

### Example 1

The rms voltage in the UK is quoted as 230 V.

Calculate the peak voltage.

$$V_{\text{rms}} = 230 \text{ V}$$

$$V_{\text{p}} = ?$$

$$\begin{aligned} V_{\text{peak}} &= \sqrt{2} \times V_{\text{rms}} \\ &= \sqrt{2} \times 230 \\ V_{\text{peak}} &= 325 \text{ V} \end{aligned}$$



# AC Current

---

An AC current also has a peak and rms value.

To calculate the rms current:

$$I_{\text{rms}} = \frac{I_{\text{peak}}}{\sqrt{2}}$$

The **rms current equals** the equivalent **dc current**.

Components in AC circuits however, must be able to withstand the peak voltage.



# AC and Ohm's Law

---

The peak or rms values can be applied to Ohm's Law.

$$V_{\text{peak}} = I_{\text{peak}} \times R$$

$$V_{\text{rms}} = I_{\text{rms}} \times R$$

## Example 1

Calculate the peak current for a  $100 \Omega$  resistor connected to a mains supply.

$$V_{\text{rms}} = 230 \text{ V}$$

$$R = 100 \Omega$$

$$I_{\text{peak}} = ?$$

$$V_{\text{peak}} = \sqrt{2} \times V_{\text{rms}}$$

$$= \sqrt{2} \times 230$$

$$\underline{\underline{V_{\text{peak}} = 325 \text{ V}}}$$

$$V_{\text{peak}} = I_{\text{peak}} R$$

$$I_{\text{peak}} = \frac{V_{\text{peak}}}{R}$$

$$= \frac{325}{100}$$

$$\underline{\underline{I_{\text{peak}} = 3.3 \text{ A}}}$$

Must use ALL peak values or ALL rms values.

You may need to use the following equations from standard grade:

$$V = IR$$

$$P = \frac{E}{t}$$


$$P = \frac{V^2}{R}$$

$$P = IV$$

$$P = I^2 R$$

When asked to calculate the **output power**, or **heat produced** (energy), you must **use rms values**.

# Peak Voltage on Oscilloscope

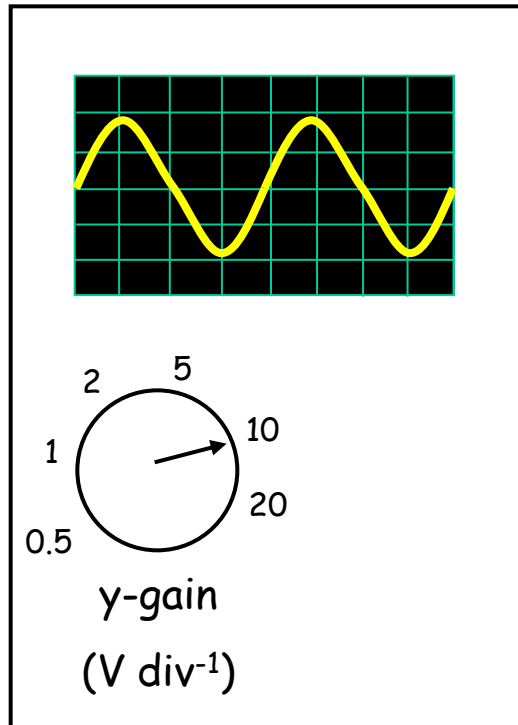

y-gain = 10 V per division

amplitude = 2 divisions


$$\begin{aligned}\text{peak voltage} &= 2 \times 10 \\ &= \underline{\underline{20\text{V}}}\end{aligned}$$

Once the peak voltage is known, the rms voltage can be calculated.

$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}} = \frac{20}{\sqrt{2}} = \underline{\underline{14.1\text{V}}}$$



# AC Frequency on Oscilloscope

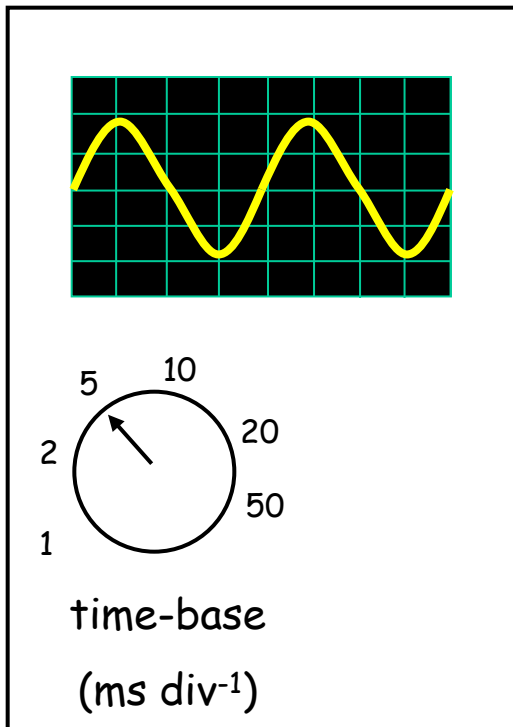

The time-base control tells you how long it takes the spot to move 1 division along the screen.

The time taken to produce **one complete wave** is the **PERIOD**.

period  
(s)

$$T = \frac{1}{f}$$

frequency  
(Hz)

One wave on the oscilloscope is 4 divisions long.


$$\begin{aligned} T &= 4 \times 5 \text{ ms} \\ &= 4 \times 5 \times 10^{-3} \\ T &= 0.02 \text{ s} \end{aligned}$$

The frequency is calculated to be:

$$\begin{aligned} f &= \frac{1}{T} \\ &= \frac{1}{0.02} \\ \underline{\underline{f = 50 \text{ Hz}}} \end{aligned}$$
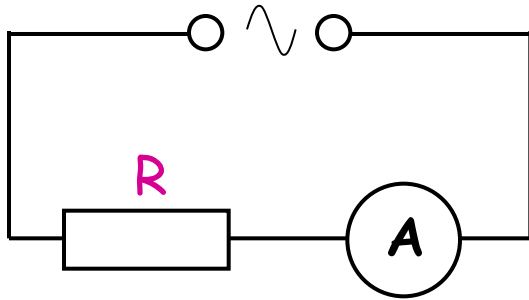
# Resistors and AC

A resistor is connected to an AC voltage supply as shown.



As the **frequency** of the AC voltage is **increased**, the **current** in the circuit is **unchanged**.

**Current is not dependent on frequency.**

A graph of current against frequency in a resistor circuit is:

