



# Unit 2 - Using Electricity

---

## 2.3 - Resistance



# Electrical Resistance

---

## Success Criteria

By the end of the lesson, you should be able to:

- △ **explain** what is meant by **resistance**.
- △ **describe** the **energy transformation** in a **resistor**.
- △ **describe** what happens to the **size of current** when:
  - resistance is **increased**
  - resistance is **decreased**

Every electrical component has resistance.

**Resistance** is how **difficult** electric charges (a current) find it **to move** around a circuit.

A **high resistance** means the electric charges will find it difficult to move.

A **low resistance** means the electric charges will find it easy to move.

So when the resistance in the circuit increases, the current in the circuit will decrease, because the charges find it more difficult to move.

## Resistors

A **resistor** is an electrical component that makes it **harder** for electric **charges** (a current) to **flow**.

The **circuit symbol** for a resistor is: 

The **energy transformation** that takes place in a resistor is:

**electrical** → **heat**



# Current and Voltage

---


## Success Criteria

By the end of the lesson, you should be able to:

- △ **name** the appropriate devices used to **measure current** and **measure voltage**.
- △ **draw** and **identify** the circuit symbols for:
  - **an ammeter**
  - **a voltmeter**
- △ **draw** a circuit diagram to show the **correct positions** of an **ammeter** and **voltmeter** in a circuit.

## Measuring Current and Voltage


The device used to **measure current** is an ammeter, and has the circuit symbol: 

To **measure voltage**, a device called a voltmeter is used which has the circuit symbol: 
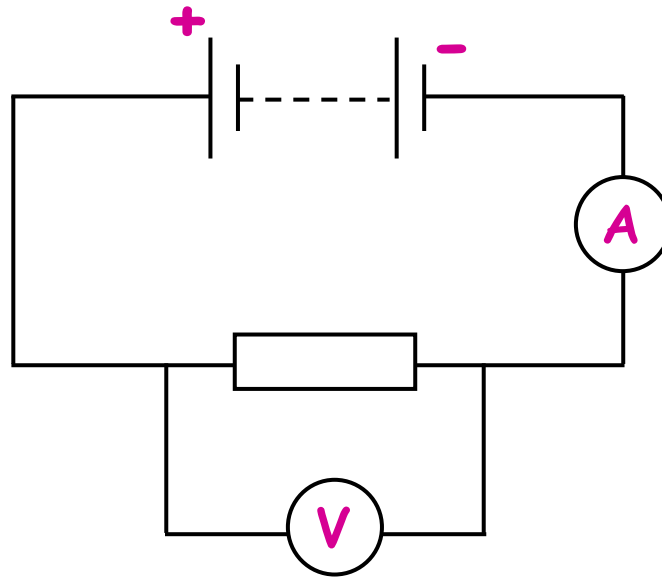
## Ammeters and Voltmeters

**Ammeters** must always be placed in **series** (current through ammeter).

A **voltmeter** must always be in **parallel** (voltage across).





# Measuring Resistance

---

## Success Criteria

By the end of the lesson, you should be able to:


- △ **explain** an experiment to **measure resistance** to include:
  - a **list** of all **measurements** made
  - the **devices used** to take each measurement
  - how the **measurements** allow you to **calculate resistance**.
- ◇ **state** for a resistor, how **voltage ÷ current** compares for **different values for current**.
- △ **state** the equation that relates **current, voltage** and **resistance**.



## Aim

To measure the resistance of a known resistor.

## Circuit Diagram

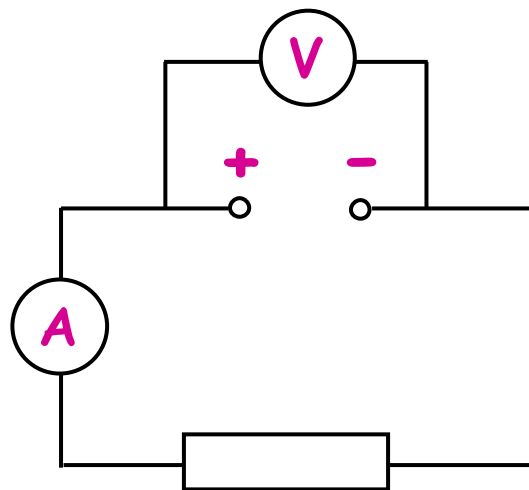

## Results

Current ( A )	Voltage ( V )	$\frac{\text{voltage}}{\text{current}}$

## Conclusion

The equation relating current, voltage and resistance is:

$$\text{resistance} = \frac{\text{voltage}}{\text{current}}$$

## Method

This must include:

- a list of all measurements made
- the devices used to make each measurement
- how the measurements allowed you to calculate resistance



# Ohm's Law

---

## Success Criteria

By the end of the lesson, you should be able to:


△ **carry out calculations** using the relationship:  $V = I R$

△ **use** correctly the unit:

➤ **ohms**

Equation

$V = I R$

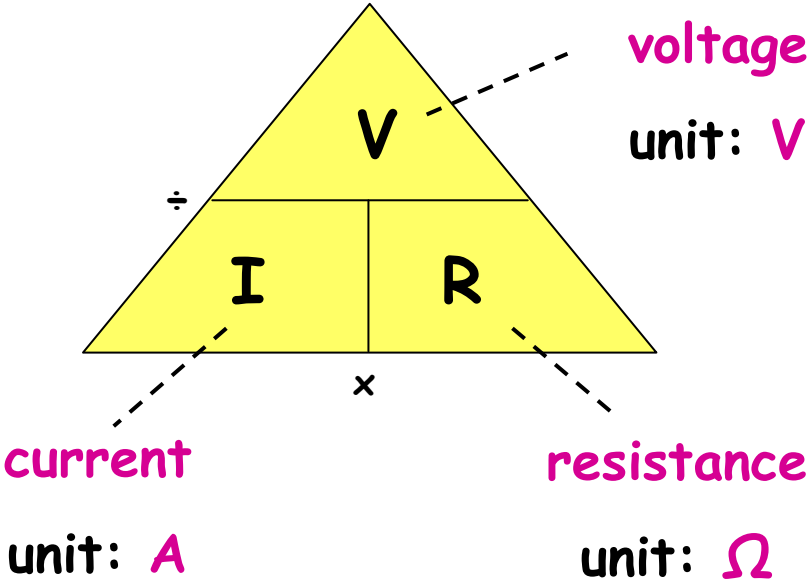

## History

Ohm's Law is named after a physics teacher called Georg Ohm.

Can you guess what nationality he was?



Brandenburg  
Gate



Bratwurst  
Sausage



Andreas  
Hinkel



German  
Flag



### Example 1

A  $100 \Omega$  resistor is connected to a  $12 \text{ V}$  battery.

Calculate the size of the current that flows through the resistor.

$$R = 100 \Omega$$

$$V = 12 \text{ V}$$

$$I = ?$$

$$I = \frac{V}{R}$$

$$= \frac{12}{100}$$

$$\underline{\underline{I = 0.12 \text{ A}}}$$

## Example 2

The heating coil of a mains electric kettle uses a current of 2.5 A.  
Calculate the resistance of the heating coil.

$$I = 2.5 \text{ A}$$

$$V = 230 \text{ V}$$

voltage is 230 V as kettle  
uses mains voltage

$$R = ?$$

$$R = \frac{V}{I}$$

$$= \frac{230}{2.5}$$

$$\underline{\underline{R = 92 \Omega}}$$



## Questions

m = milli ( $\times 10^{-3}$ )

k = kilo ( $\times 10^3$ )

$\mu$  = micro ( $\times 10^{-6}$ )

M = mega ( $\times 10^6$ )

	<u>voltage</u>	<u>current</u>	<u>resistance</u>
1.	20 V	2.5 A	
2.		5 A	100 $\Omega$
3.	125 V		25 $\Omega$
4.		10 mA	6 M $\Omega$
5.	2.4 kV	0.08 mA	



# Variable Resistors

---


## Success Criteria

By the end of the lesson, you should be able to:

- △ **describe** the **size of current** in a circuit when a variable resistor has:
  - a **high resistance**
  - a **low resistance**
- △ **state** some practical **uses** of **variable resistors**.

A variable resistor can alter the size of current in a circuit.

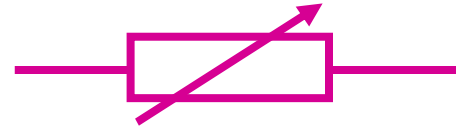
The circuit symbol for a variable resistor is:



## Aim

Identify what happens to the size of current when resistance of variable resistor is changed.

## Circuit Diagram

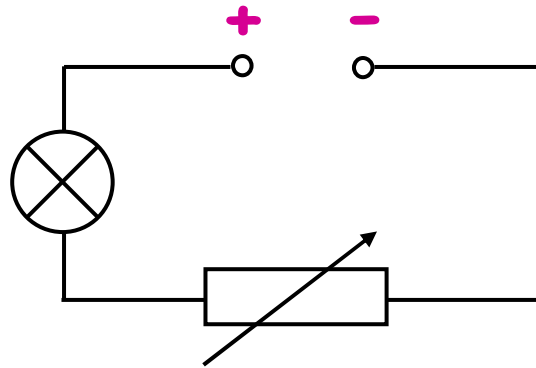

## Results

resistance	brightness of bulb	current
LOW	BRIGHT	HIGH
HIGH	DULL	LOW

## Conclusion

When the resistance of a variable resistor is increased, the current in the circuit decreases.

## Practical Uses of Variable Resistors

Variable resistors are used in:

- **dimmer switches** for a light
- **volume controls** in a stereo
- **speed control** in a remote controlled car
- **petrol gauges** to show fuel level
- **temperature control** in an oven



# Types of Lamp

---

## Success Criteria

By the end of the lesson, you should be able to:

- △ **state** examples of resistive circuits that **transform electrical** energy into **heat**.
- △ **state** the **full energy transformation** that takes place in a **lamp**.
- △ **state where** the **energy is transformed** in
  - a **filament lamp**
  - a **discharge tube**
- △ **state** and **explain** which type of **lamp** is **most efficient**.

## Current in Wires

When an **electric current** flows through a **wire**, **electrical** energy is transformed into **other forms** of energy.

## Resistive Circuits at Home

A resistive circuit changes **electrical** energy to **heat**.

This happens in **electric fires**, **cookers** and **kettles**.


## Lamps

In a **lamp**, electrical energy is changed into **light** and **heat**.



## Filament Lamps

metal  
resistance  
wire  
(filament)

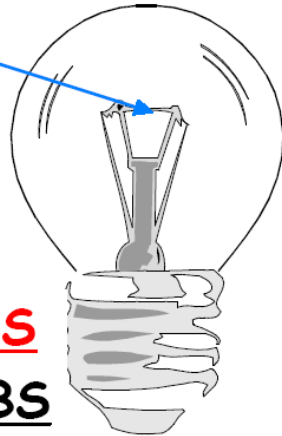

FILAMENT LAMPS  
e.g., LIGHT BULBS


The **energy change** takes place in the **metal resistance wire** known as the filament.

A **lot of heat** is produced.

## Discharge Tube

The **energy change** occurs in the **gas** inside a sealed tube.

**Very little heat** is produced.

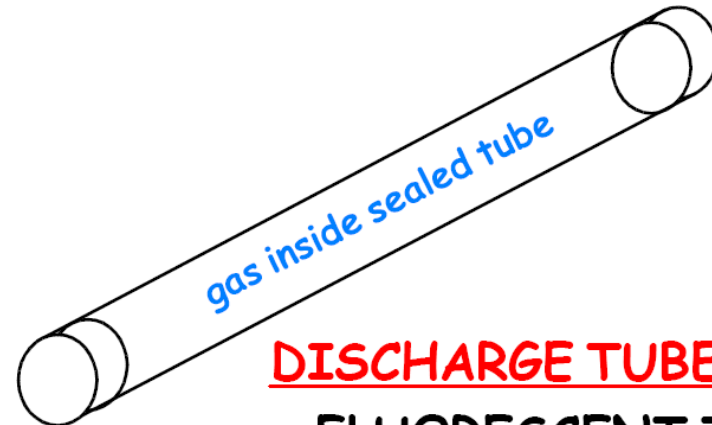

DISCHARGE TUBES  
e.g., FLUORESCENT TUBES

## Efficiency

Discharge tubes are MORE efficient than filament lamps because more energy is transferred into light with less electrical energy transferred to heat.



filament lamp



discharge tube



Powered by DIYTrade.com

**energy saving bulbs  
(discharge tubes)**



	<u>Filament Lamp</u>	<u>Discharge Tube</u>
Also Known As	light bulb	fluorescent tube
Energy Transformation	electrical → light + heat	electrical → light + heat
Energy Change Takes Place	in filament	in the gas
Most Efficient	No A lot of heat energy produced.	Yes More electrical energy transferred to light.
Most expensive to operate	yes	no



# Measuring Power

---

## Success Criteria

By the end of the lesson, you should be able to:

- △ **explain** an experiment to **measure power** to include:
  - a **list** of all **measurements** made
  - the **devices used** to take each measurement
  - how the **measurements** allow you to **calculate electrical power**.

## Aim

To find the power of a light bulb.

## Results

power rating (W)	energy (J)	time (s)	$\frac{\text{energy}}{\text{time}}$
24	563	20	28
36	669	20	33
48	890	20	44

## Conclusion

Electrical power is the energy used divided by the time an appliance is switched on for.

$$\text{power} = \frac{\text{energy}}{\text{time}}$$

## Method

This must include:

- a list of all measurements made
- the devices used to make each measurement
- how the measurements allowed you to calculate power



# Power, Energy and Time

---

## Success Criteria


By the end of the lesson, you should be able to:

- △ **state** the relationship between **power**, **energy** and **time**.
- △ **carry out calculations** using the relationship between **power**, **energy** and **time**.
- △ **use** correctly the unit:
  - **joules**
  - **watts**



## Equation

$$P = \frac{E}{t}$$

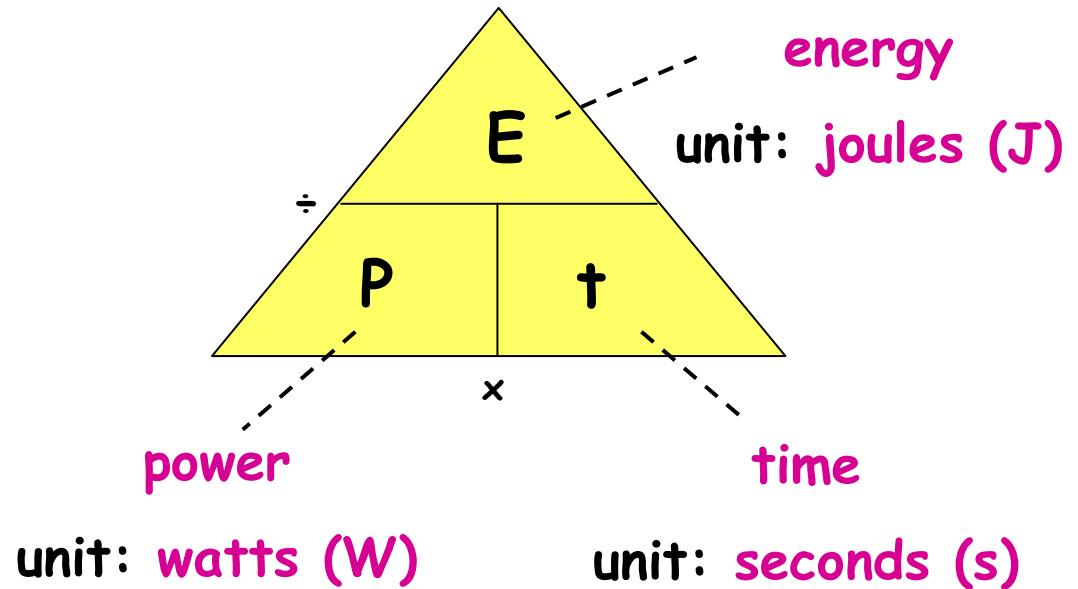

1 watt = 1 joule per second

A 60 W light bulb uses 60 joules of energy per second.

A 150 W television uses 150 joules of energy per second.

A 2 kW kettle uses 2000 joules of energy per second.

## Example 1

A 100 W television is switched on for 30 minutes.  
Calculate how much energy it uses in this time.

$$P = 100 \text{ W}$$

$$\begin{aligned} t &= 30 \text{ min} \\ &= 30 \times 60 \\ &= 1800 \text{ s} \end{aligned}$$

$$E = ?$$

$$E = P t$$

$$= 100 \times 1800$$

$$= 180\,000 \text{ J}$$

$$\underline{\underline{E = 180 \times 10^3 \text{ J}}}$$

## Example 2

A 100 W light bulb is left on and uses 54 kJ of energy.  
Calculate how long the light bulb was on.

$$P = 100 \text{ W}$$

$$E = 54 \text{ kJ} \\ = 54 \times 10^3 \text{ J}$$

$$t = ?$$

$$t = \frac{E}{P}$$

$$= \frac{54 \times 10^3}{100}$$

$$\underline{\underline{t = 540 \text{ s}}}$$

## Questions

m = milli ( $\times 10^{-3}$ )

k = kilo ( $\times 10^3$ )

$\mu$  = micro ( $\times 10^{-6}$ )

M = mega ( $\times 10^6$ )

	<u>power</u>	<u>time</u>	<u>energy</u>
1.	60 W	4 min	14 400 J
2.	200 W	5 min	60 kJ
3.	25 mW	600 s	15 J
4.	80 W	$3 \times 10^{-3}$ s	0.24 J
5.	1.3 kW	720 s	935 000 J



# Power, Current and Voltage

---


## Success Criteria

By the end of the lesson, you should be able to:

- △ **state** the relationship between **power**, **current** and **voltage**.
- △ **carry out calculations** using the relationship between **power**, **current** and **voltage**.

## Equation

$$P = I V$$

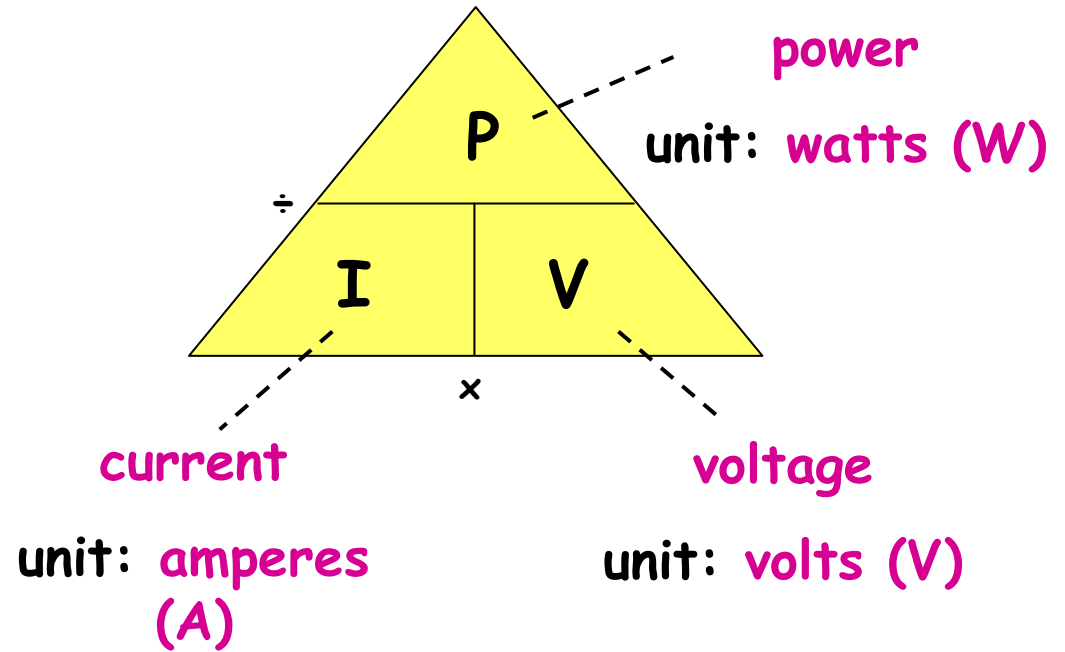

## Example 1

A heater connected to the mains supply draws 20 A.

(a) Calculate the power rating of this heater.

$$V = 230 \text{ V}$$

$$I = 20 \text{ A}$$

$$P = ?$$

$$P = I V$$

$$= 230 \times 20$$

$$\underline{\underline{P = 4600 \text{ W}}}$$

(b) How many joules of energy does the heater use per second.

$$\boxed{1 \text{ watt} = 1 \text{ joule per second}}$$

So the heater uses 4600 joules of energy per second.

## Example 2

A 1 kW electric saw is used from the mains supply.  
Calculate the size of current the saw uses.

$$\begin{aligned} P &= 1 \text{ kW} \\ &= 1 \times 10^3 \text{ W} \end{aligned}$$

$$V = 230 \text{ V}$$

**\*\* mains voltage \*\***

$$I = ?$$

$$\begin{aligned} I &= \frac{P}{V} \\ &= \frac{1 \times 10^3}{230} \\ I &= \underline{\underline{4.3 \text{ A}}} \end{aligned}$$



## Questions


m = milli ( $\times 10^{-3}$ )

k = kilo ( $\times 10^3$ )

$\mu$  = micro ( $\times 10^{-6}$ )

M = mega ( $\times 10^6$ )

	<u>current</u>	<u>voltage</u>	<u>power</u>
1.	3 A	5 V	15 W
2.	15 A	230 V	3.45 kW
3.	25 mA	2 kV	50 W
4.	6 $\mu$ A	2000 V	12 mW
5.	2 A	15 mV	0.03 W

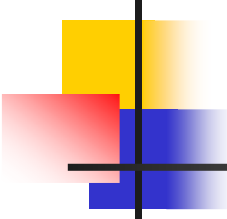

# Combining $P=IV$ and $V=IR$

---

## Success Criteria

By the end of the lesson, you should be able to:

- ◇ *show how  $P=IV$  and  $V=IR$  can be combined to produce two new equations.*
- ◇ *carry out calculations using the relationship between power, current and resistance.*
- ◇ *carry out calculations using the relationship between power, voltage and resistance.*

## Power, Current and Resistance

Consider the equations:

$$V = I \times R$$

and

$$P = I \times V$$

Start with:

$$P = I \times V$$

But:


$$V = I \times R$$

$$P = I \times I \times R$$

So we get:

$$P = I^2 \times R$$

$$P = I^2 \times R$$

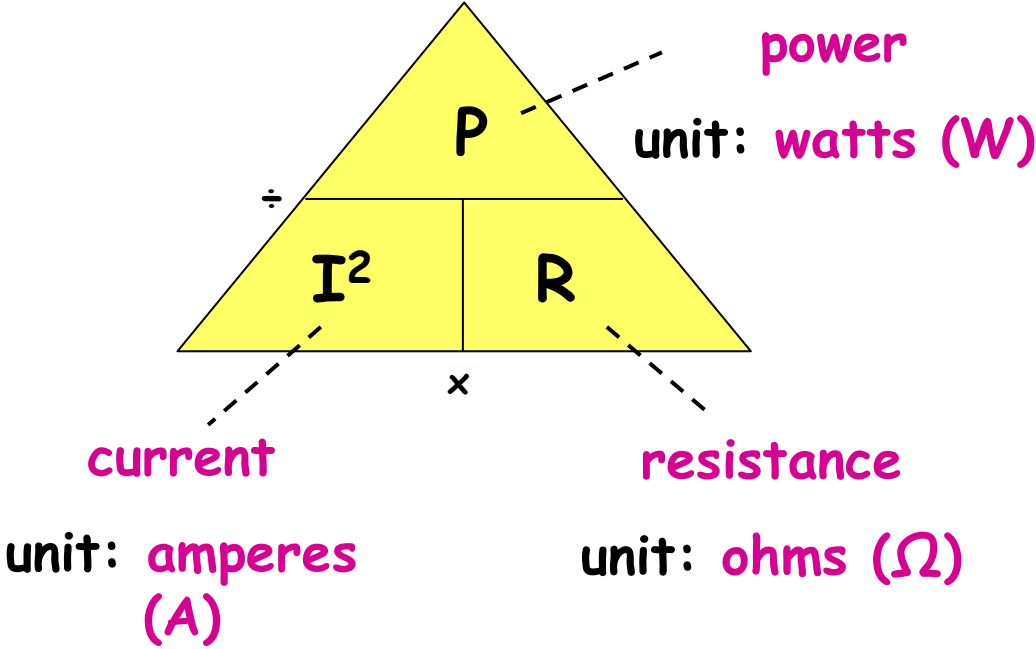

## Example

An electric drill has a power rating of 460 W. Whilst in operation, the drill has a resistance of 115  $\Omega$ . What is the current passing through the drill?

$$P = 460 \text{ W}$$

$$R = 115 \Omega$$

$$I = ???$$

$$I^2 = \frac{P}{R}$$

$$= \frac{460}{115}$$

$$I^2 = 4$$

$$I = \sqrt{4}$$

$$\underline{\underline{I = 2 \text{ A}}}$$

# Power, Voltage and Resistance

Consider the equations:

$$I = \frac{V}{R}$$

and

$$P = I \times V$$

Start with:

$$P = I \times V$$

But:


$$I = \frac{V}{R}$$

$$P = \frac{V}{R} \times V$$

So we get:

$$P = \frac{V^2}{R}$$

$$P = \frac{V^2}{R}$$

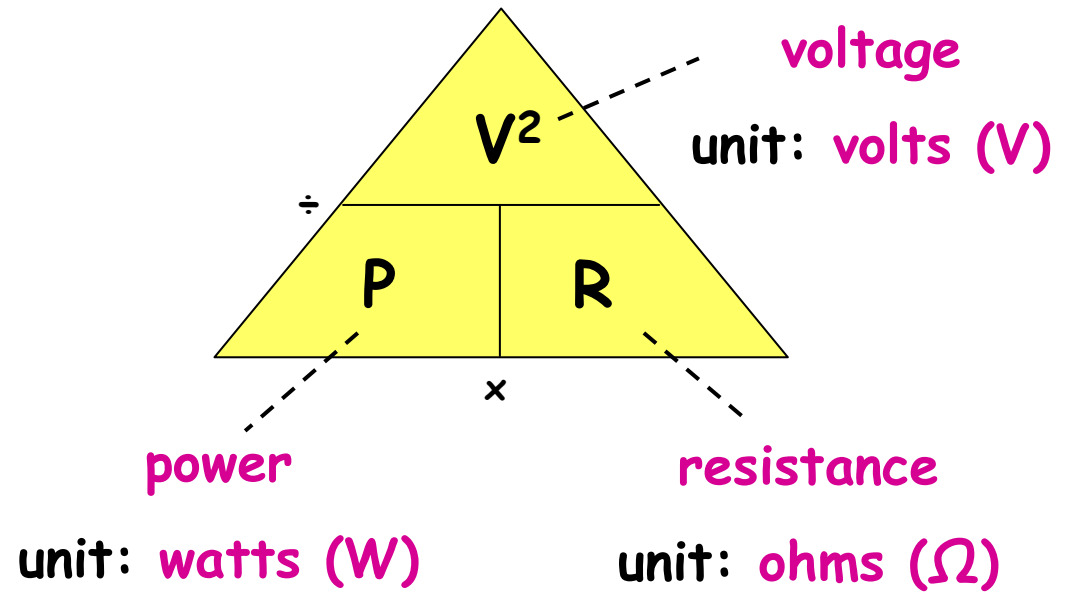

## Example

A lamp has a power of 36 W and a resistance of  $4\Omega$ .  
What voltage should it be connected to?

$$P = 36 \text{ W}$$

$$R = 4 \Omega$$

$$V = ???$$

$$V^2 = P \times R$$
$$= 36 \times 4$$

$$V^2 = 144$$

$$V = \sqrt{144}$$

$$\underline{\underline{V = 12 \text{ V}}}$$



## Questions

m = milli ( $\times 10^{-3}$ )

k = kilo ( $\times 10^3$ )

$\mu$  = micro ( $\times 10^{-6}$ )

M = mega ( $\times 10^6$ )

	<u>power</u>	<u>current</u>	<u>resistance</u>
1.	40 W	2 A	10 $\Omega$
2.	6 mW	5 $\mu$ A	$240 \times 10^6 \Omega$
3.	5.76 kW	2.4 A	1 k $\Omega$

	<u>power</u>	<u>voltage</u>	<u>resistance</u>
4.	25 000 W	5 kV	1 000 $\Omega$
5.	16 kW	40 000 V	0.1 M $\Omega$
6.	640 mW	800 V	1 000 k $\Omega$